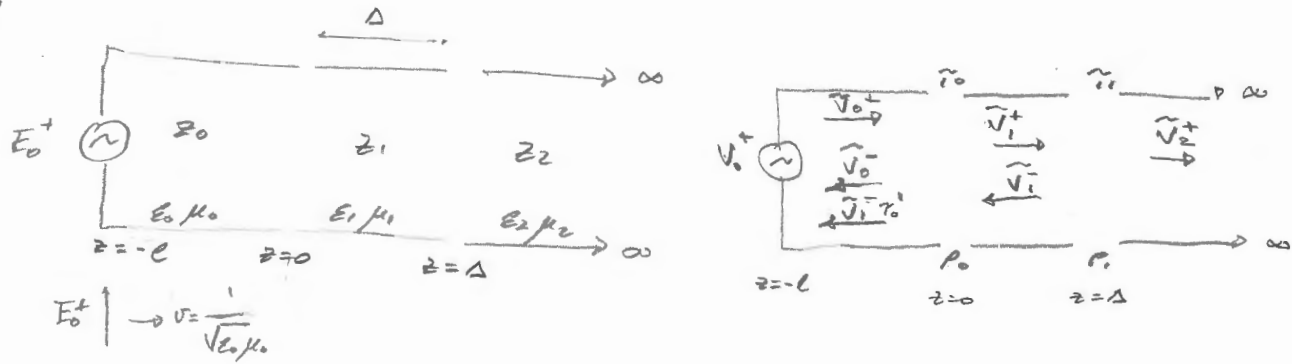


## 9.2 Multiple Impedances

9.2.1



$$\tilde{V}_n(z) = \tilde{V}_n^+ e^{-j\beta_n z} + \tilde{V}_n^- e^{+j\beta_n z} \Rightarrow V_n(z, t) = \text{Re} [\tilde{V}_n(z) e^{j\omega t}]$$

$V_0^+$  is known and  $V_2^- = 0$ ; Find  $\tilde{V}_0^-(z), \tilde{V}_1^+(z), \tilde{V}_1^-(z)$  and  $\tilde{V}_2^+(z)$

$$\beta_0 = \frac{\omega}{v_0} = \omega \sqrt{\epsilon_0 \mu_0}; \quad \beta_1 = \omega \sqrt{\epsilon_1 \mu_1}, \quad \beta_2 = \omega \sqrt{\epsilon_2 \mu_2}$$

$$\tilde{V}_0(z) = \tilde{V}_0^+ e^{-j\beta_0 z} + \tilde{V}_0^- e^{+j\beta_0 z} \quad \text{and} \quad \rho_0 = \frac{z_1 - z_0}{z_1 + z_0} \quad (\text{from 5.7 (8)})$$

$$\Rightarrow \tilde{V}_0^- = \tilde{V}_0^+ \rho_0 e^{+j\beta_0 z} \quad \text{at } z=0 \Rightarrow \tilde{V}_0(z) = \tilde{V}_0^+ \rho_0 = \tilde{V}_0^+ \left( \frac{z_1 - z_0}{z_1 + z_0} \right) e^{+j\beta_0 z}$$

$$\tilde{V}_1^+ = \tilde{V}_0^+ \tau_0 e^{-j\beta_1 z} \Rightarrow \text{for } \tau_0 = \frac{2z_1}{z_1 + z_0} \quad \text{from 5.7 (9)}$$

$$\text{at } z=1 \quad \tilde{V}_1(z) = \tilde{V}_0^+ \tau_0 e^{-j\beta_1 z}$$

$$\Rightarrow \text{at } z=\Delta \quad \tilde{V}_1(\Delta) = \tilde{V}_0^+ \tau_0 e^{-j\beta_1 \Delta} = \tilde{V}_0^+ \left( \frac{2z_1}{z_1 + z_0} \right) e^{-j\beta_1 \Delta}$$

$$\text{for } \tilde{V}_1^- = \tilde{V}_1^+ \rho_1 e^{+j\beta_1 \Delta} \quad \text{and} \quad \rho_1 = \frac{z_2 - z_1}{z_2 + z_1} \quad \text{and at } z=\Delta$$

$$\Rightarrow \tilde{V}_1^-(z) = \tilde{V}_0^+ \left( \frac{2z_1}{z_1 + z_0} \right) \left( \frac{z_2 - z_1}{z_2 + z_1} \right) e^{+j\beta_1 z}$$

$$\text{at } z=\Delta \Rightarrow \tau = \frac{2z_2}{z_2 + z_1} \quad \text{and at } z=\Delta+1 \Rightarrow$$

$$\Rightarrow \tilde{V}_2^+(z) = \tilde{V}_1^+ \tau e^{+j\beta_2(\Delta+1)} = \tilde{V}_0^+ \left( \frac{2z_1}{z_1 + z_0} \right) \left( \frac{2z_2}{z_2 + z_1} \right) e^{+j\beta_2 z}$$

$$\tilde{V}_2^- = 0 \quad \tau_0' = \frac{v_L}{v_-} = \frac{2z_1}{z_1 - z_0}$$

$$\text{Recalculate } \tilde{V}_0^- = \tilde{V}_0^-(0) + \tilde{V}_1^-(\Delta) \tau_0' = \tilde{V}_0^+ \left( \frac{z_1 - z_0}{z_1 + z_0} \right) e^{+j\beta_0 z} + \tilde{V}_0^+ \left( \frac{2z_1}{z_1 + z_0} \right) \left( \frac{z_2 - z_1}{z_2 + z_1} \right) \left( \frac{2z_1}{z_1 - z_0} \right) e^{+j\beta_1 z}$$

Find  $\frac{\tilde{V}_0^-(z)}{\tilde{V}_0^+(z)}, \frac{\tilde{V}_1^-(z)}{\tilde{V}_1^+(z)}$

$$\frac{\tilde{V}_0^-(z)}{\tilde{V}_0^+(z)} = \frac{\cancel{\tilde{V}_0^+} \left( \frac{z_1 - z_0}{z_1 + z_0} \right) e^{j\beta_0 z} + \cancel{\tilde{V}_0^+} \left( \frac{z_2 z_1}{z_1 + z_0} \right) \left( \frac{z_2 - z_1}{z_2 + z_1} \right) \left( \frac{z_2 z_1}{z_1 - z_0} \right) e^{j\beta_1 z}}{\cancel{\tilde{V}_0^+} e^{-j\beta_0 z}} =$$

$$= \frac{z_1 - z_0}{z_1 + z_0} e^{2j\beta_0 z} + \left( \frac{z_2 z_1}{z_1 + z_0} \right) \left( \frac{z_2 - z_1}{z_2 + z_1} \right) \left( \frac{z_2 z_1}{z_1 - z_0} \right) e^{jz(\beta_0 + \beta_1)} =$$

$$= \rho_0 e^{2j\beta_0 z} + \tau_0 \rho_1 \tau_0' e^{jz(\beta_0 + \beta_1)}$$

$$\frac{\tilde{V}_1^-(z)}{\tilde{V}_1^+(z)} = \frac{\cancel{\tilde{V}_0^+} \left( \frac{z_2 z_1}{z_1 + z_0} \right) \left( \frac{z_2 - z_1}{z_2 + z_1} \right) e^{j\beta_1 z}}{\cancel{\tilde{V}_0^+} \left( \frac{z_2 z_1}{z_1 + z_0} \right) e^{-j\beta_1 z}} = \left( \frac{z_2 - z_1}{z_2 + z_1} \right) e^{2j\beta_1 z} = \rho_1 e^{2j\beta_1 z}$$

9.2.2 •  $V(z, t) = V^+ [\cos(\omega t - \beta z) + \rho \cos(\omega t + \beta z)]$

1.  $V(z, t) = A \cos \omega t \cos \beta z + B \sin \omega t \sin \beta z \Rightarrow$  find A and B

$$V^+ \cos(\omega t - \beta z) = V^+ \cos \omega t \cos \beta z + V^+ \sin \omega t \sin \beta z$$

$$V^+ \rho \cos(\omega t + \beta z) = V^+ \rho \cos \omega t \cos \beta z - V^+ \rho \sin \omega t \sin \beta z$$


$$V(z, t) = V^+ \cos(\omega t - \beta z) + V^+ \rho \cos(\omega t + \beta z) =$$

$$= V^+ \cos \omega t \cos \beta z + V^+ \sin \omega t \sin \beta z + V^+ \rho \cos \omega t \cos \beta z - V^+ \rho \sin \omega t \sin \beta z =$$

$$= V^+(1+\rho) \cos \omega t \cos \beta z + V^+(1-\rho) \sin \omega t \sin \beta z \Rightarrow$$

$$A = V^+(1+\rho) \quad \text{and} \quad B = V^+(1-\rho) \Rightarrow$$

$$\Rightarrow A \cos \omega t \cos \beta z + B \sin \omega t \sin \beta z$$

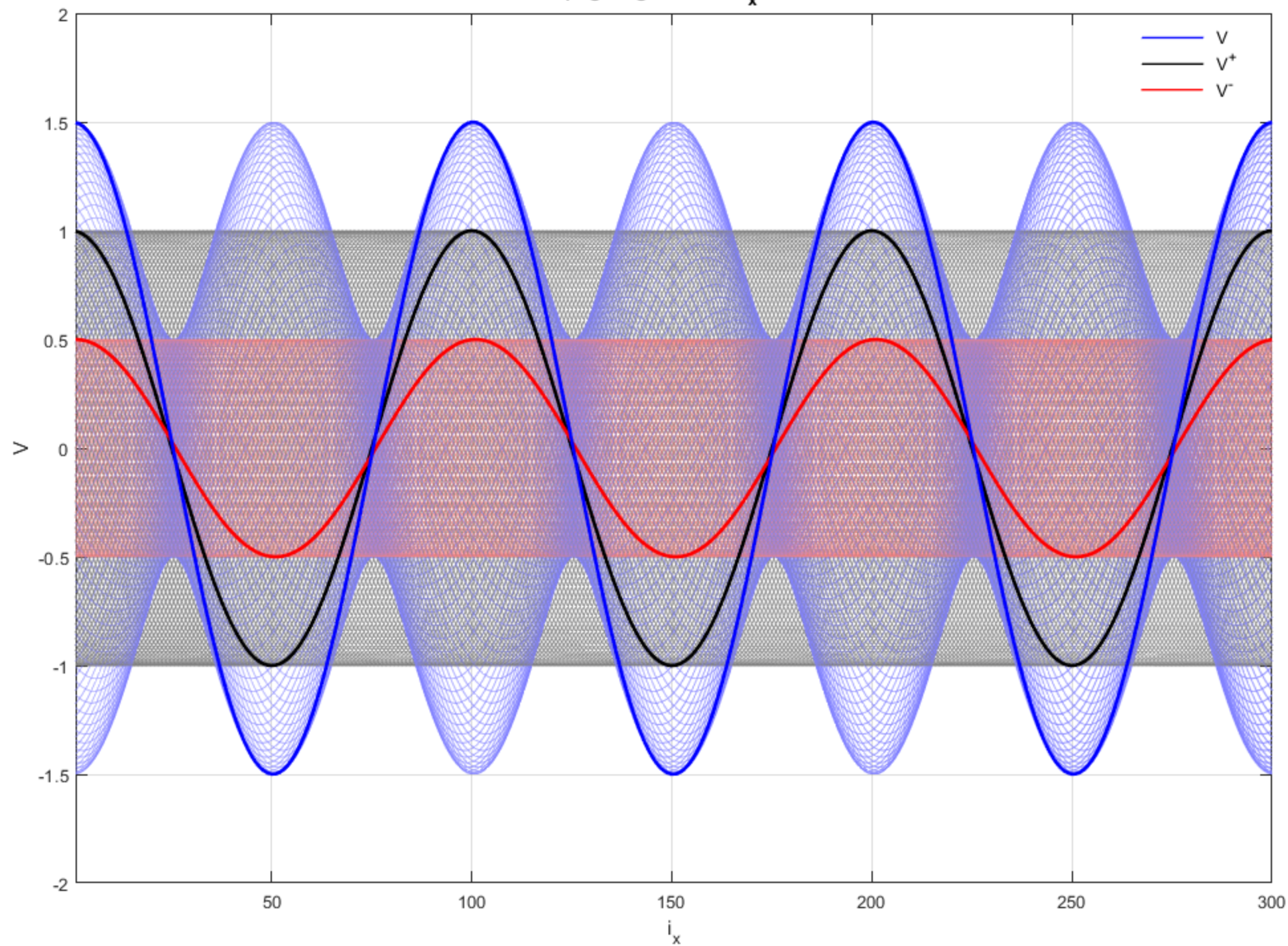2.  $i_x = 300$ Propagating Waves at  $i_x = 300$ 

3. By plotting a  $V^- = 1/2$  traveling to the left, we are replotting the reflected wave at  $x = 300$ . When we add  $V^+ = 1$  and  $V^- = 0.5$  we can observe the  $V_{max} = 1.5$  and  $V_{min} = 0.5$  created in that wave (blue in my plot). From this  $V_{max}$  and  $V_{min}$ , we can obtain the Voltage Wave Standing Ratio (VSWR) by

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1.5}{0.5} = 3$$

Likewise, we could obtain the magnitude of the reflection coefficient  $\rho$  by

$$|\rho| = \frac{S-1}{S+1} = \frac{2}{4} = 0.5$$

However, just from the plot is difficult to calculate  $\theta_p$  to obtain  $\rho = |\rho|e^{j\theta_p}$ , but an attempt looking at  $V_{min}$  from  $x = 300$  looks like at  $x = 275$ , or  $(0.25\lambda)$  and


$$\theta_p = 2\beta(0.25\lambda) - \pi \quad ; \quad \text{for } \beta = \frac{\omega}{c} = \frac{2\pi f}{c} = \frac{2\pi}{\lambda}$$

$$\theta_p = 4\pi(0.25) - \pi = 0$$

This confirms the lack of phase difference in  $V^+$  and  $V^-$  across the plot, and:

$$\rho = |\rho| = \frac{1}{2}$$

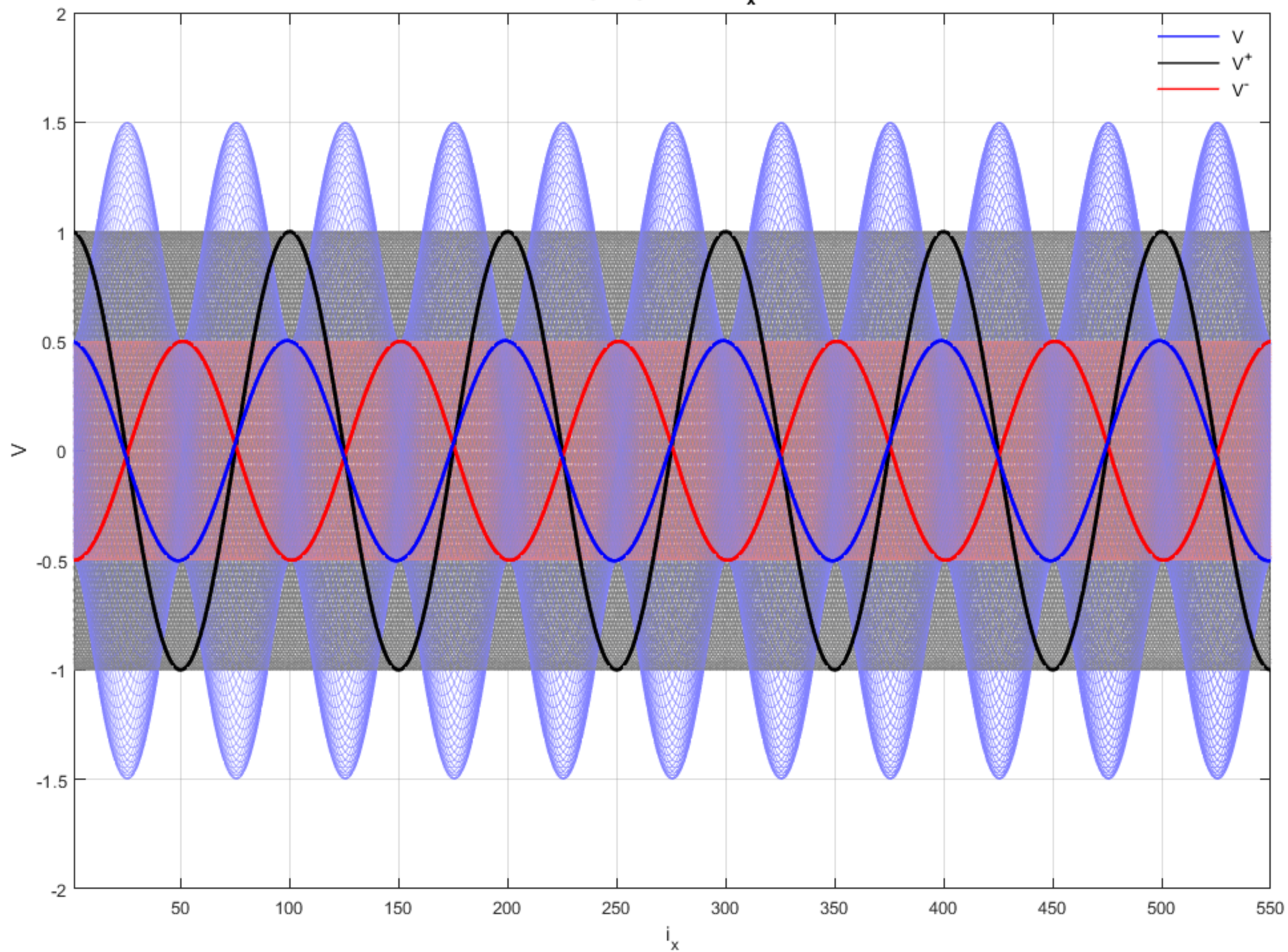

Propagating Waves at  $i_x = 550$ 

4. From the plot, and as before in 3.

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1.5}{0.5} = 3$$

$$|p| = \frac{S-1}{S+1} = 0.5$$

however, with  $x = 550$ ,  $\theta_p$  has changed, and  $V_{min}$  is at  $x = 500$  or  $(0.5\lambda)$ , therefore

$$\theta_p = 2\beta(0.5\lambda) - \pi = \pi$$

which seems about right when comparing  $V^+$  and  $V^-$  that show about  $180^\circ$  difference.